

# Cache Controller Implementation with Write-Through Policy

Group no.10

**Group Members:**

Name	Track
Ehab Mostafa Farghly	Design
Mohamed Mahmoud Elfeki	Verification

# Top level architecture of RISC V with cache memory

412

CHAPTER SEVEN Microarchitecture

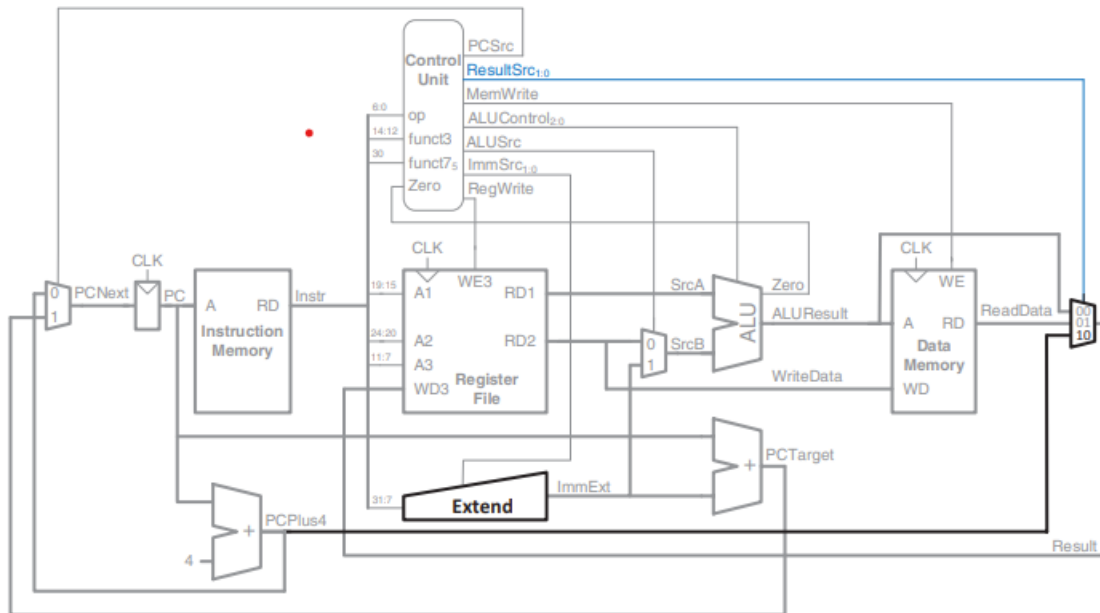


Figure 7.15 Enhanced datapath for jal

Figure 1 RISC-v Architecture

## Comments:

- Only change we did on RISC-v that we replaced Data Memory Block by our Implementation of Cache Memory.
- The main difference between this architecture and the architecture with cache memory that data memory has 2 more signals **stall** and **memory read**.
- stall signal is output from Cache Memory Block and input to the PC. If its value equal 1 it will stall PC and prevent it from incrementing and taking following instructions.
- Memory Read will come from control unit and gives value 1 only when the opcode is LW Instruction.

## Top level architecture of cache memory

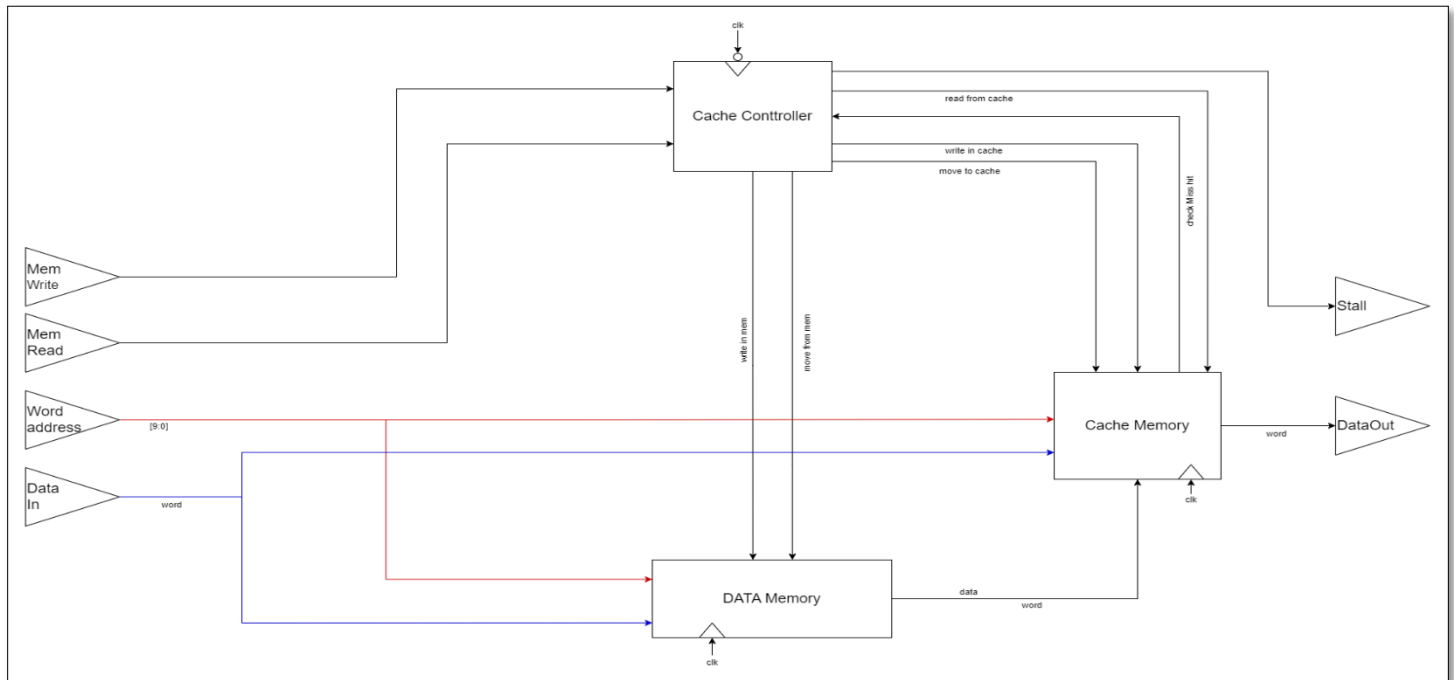


Figure 2 Cache Memory Block Diagram

### Comments:

- This is the Block Diagram representing our implementation of the cache controller.
- DATA Memory & Cache Memory works at the Positive edge clk .
- Cache Controller works at the negative edge clk.
- So, we can consider All Architecture works at negedge clk of RISC-v because the Controller is the brain of the design.

# Cache Controller FSM

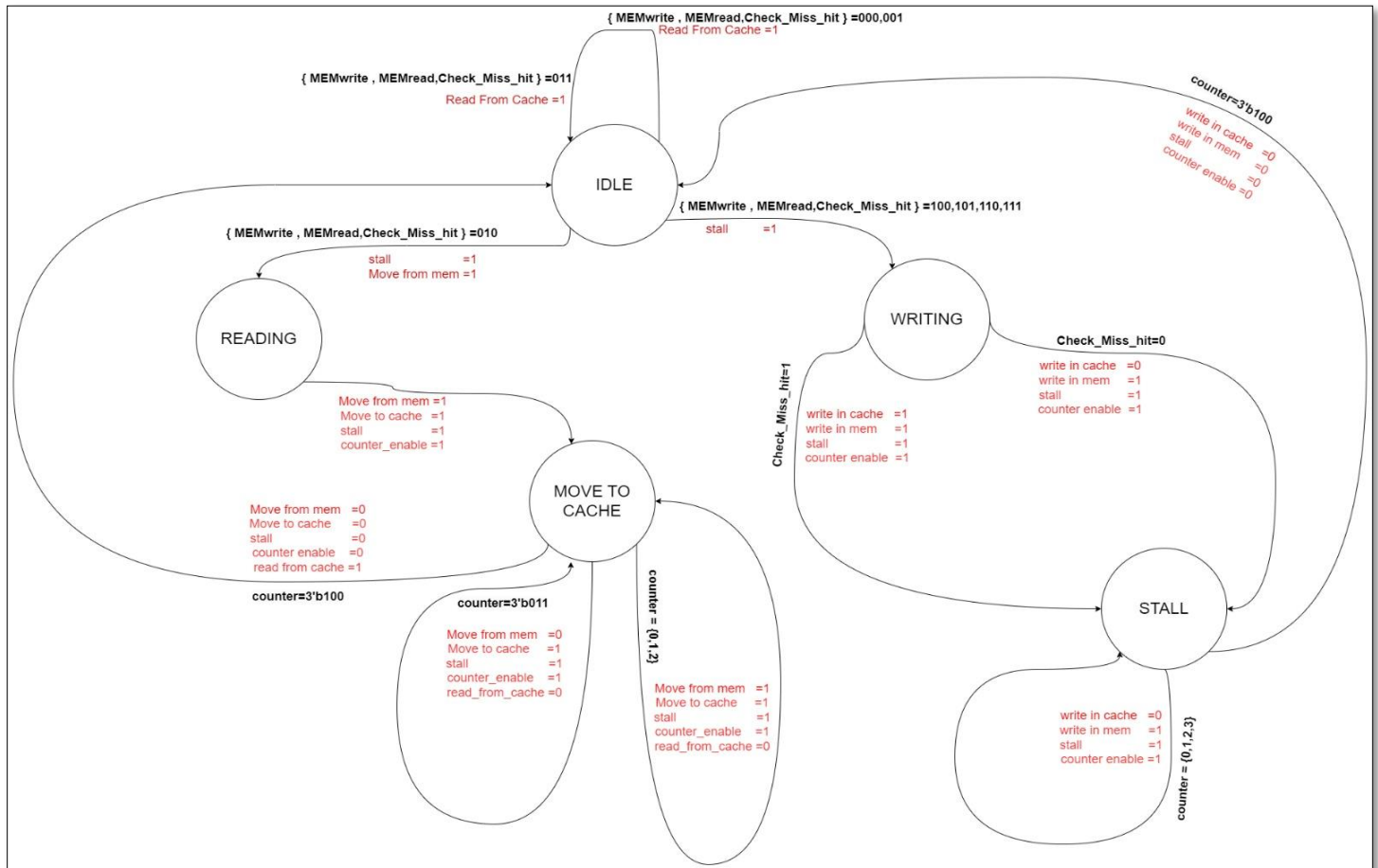


Figure 3 Cache Controller FSM

## Simulation Testcases & Results

- Test cases of cache memory

```

/***** testcases *****/
*****/

/* scenario writing in block and check the reading operations of them miss first then
all hit */
/** write operations **/

write_data('b111_00010_01', 'd16');
write_data('b111_00010_10', 'd8');
write_data('b111_00010_00', 'd4');
write_data('b111_00010_11', 'd2');

/** read operations **/

```

```

read_data ('b111_00010_11);
read_data ('b111_00010_10);
read_data ('b111_00010_01);
read_data ('b111_00010_00);

/* scenario writing in block exist in cache and check the writing operations of them
hit and store in cache and memory in same time */
/** write operations **/

write_data('b111_00010_01 ','d100 ');
write_data('b111_00010_10 ','d120 ');

/** read operations **/

read_data ('b111_00010_00);
read_data ('b111_00010_01);
read_data ('b111_00010_10);
read_data ('b111_00010_11);

/* scenario addressing same block different in tag with different values */
/** write operations **/

write_data('b101_00010_01 ','d200 ');
write_data('b101_00010_10 ','d220 ');

/** read operations **/

read_data ('b101_00010_00);
read_data ('b101_00010_01);
read_data ('b101_00010_10);
read_data ('b111_00010_11);
read_data ('b111_00010_01);

/***** Random processes *****/
/** write operations **/

write_data('b000_00110_01 ','d60 '); // Block 6 tag =0 ofsset=1
write_data('b011_01010_01 ','d100 '); // Block 10 tag =3 offset=1
write_data('b010_00111_01 ','d20 '); // Block 2 tag=2 offset=1
write_data('b110_10010_10 ','d60 '); // Blcok
18 tag=6 offset=2 /***/
write_data('b000_01011_00 ','d110 '); // Block 11 tag =0 offset=0
write_data('b101_10010_11 ','d200 '); // Block 18 tag=5 offset=3
write_data('b001_00000_11 ','d1000); // Block 0 tag =1 offset=3
write_data('b001_10011_01 ','d190 '); // Block 19 tag =1 offset=1
write_data('b111_11010_10 ','d260 '); // Block 26 tag =7 offset=2

```

```
/** read operations **/
```

```
read_data ('b000_00110_01);
read_data ('b011_01010_01);
read_data ('b010_00111_01);
read_data ('b110_10010_10);
read_data ('b110_10010_10);
read_data ('b000_01011_00);
read_data ('b101_10010_11);
read_data ('b001_00000_11);
read_data ('b001_10011_01);
read_data ('b111_11010_10);
```

- Simulation result in this case

 


Figure 4 Cache simulation Results

 


Figure 5 Cache simulation Results



Figure 6 Cache simulation Results

 


Figure 7 Cache simulation Results

- **Test cases RISC-v integrated with Cache Memory Block**

Machine Code	Assembly Code
00F00093	addi x1 x0 15
01400113	addi x2 x0 20
01900193	addi x3 x0 25
01E00213	addi x4 x0 30
01900293	addi x5 x0 25
0020A2A3	sw x2 5(x1)
0030A323	sw x3 6(x1)
0040A3A3	sw x4 7(x1)
0050A423	sw x5 8(x1)
0050A303	lw x6 5(x1)
0060A383	lw x7 6(x1)
0070A403	lw x8 7(x1)
0080A483	lw x9 8(x1)

- **Simulation result in this case**

 


Figure 8 RISC-V with Cache memory simulation Results

Memory Data - /RISC_V_testbench/DUT/u0/u3/reg_file - Default																	
0	0	15	20	25	30	25	20	25	30	25	0	0	0	0	0	0	0
17	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
34																	

Figure 9 Reg File Memory

## Comments:

- As we see in the waveform stall signal is high five times as miss occur in all 4 times of storing and miss occur in first time of loading then hit occur and register files contain the proper results.

# RTL of the Cache Memory Controller

## Cache Controller

```
module cache_controller(  
    input  wire      clk,rst,  
    input  wire      Mem_Write,Mem_Read,  
    input  wire      check_Miss_hit,  
  
    output reg       write_in_mem,  
    output reg       write_in_cache,  
    output reg       move_from_mem,  
    output reg       move_to_cache,  
    output reg       read_from_cache,  
    output reg       stall  
);  
parameter IDLE      =3'b000,  
          READING    =3'b001,  
          MOVE_TO_CACHE =3'b010,  
          WRITING     =3'b011,  
          STALL       =3'b100;  
  
reg [2:0] current_state,next_state;  
reg [2:0] counter;  
reg      counter_enable;  
  
always @(negedge clk or negedge rst)  
begin  
    if(!rst)  
        begin  
            counter <='b0;  
        end  
    else if (counter_enable)  
        begin  
            counter <= counter +'b1;  
        end  
    else  
        begin  
            counter <= 'b0;  
        end  
end  
  
always @(negedge clk or negedge rst)  
begin  
    if(!rst)  
        begin  
            current_state <=IDLE;
```



```

        end
    else
        begin
            current_state <= next_state;
        end
    end
end

always@(*)
begin
    write_in_mem      ='b0;
    write_in_cache    ='b0;
    move_from_mem     ='b0;
    move_to_cache     ='b0;
    read_from_cache   ='b0;
    counter_enable    ='b0;

    case(current_state)
        IDLE          : begin
            if((Mem_Read=='b1) && (Mem_Write == 'b0) && (check_Miss_hit=='b1)
)
                begin
                    next_state = IDLE;
                    stall      ='b0;
                    read_from_cache='b1;
                end

            else if((Mem_Read=='b1) && (Mem_Write == 'b0) &&
(check_Miss_hit=='b0) )
                begin
                    next_state = READING;
                    stall='b1;
                    move_from_mem = 'b1;

                end

            else if((Mem_Read=='b0) && (Mem_Write == 'b1) )
                begin
                    next_state = WRITING;
                    stall='b1;

                end

            else
                begin
                    next_state =IDLE;
                    stall='b0;

                end

            end

        end

        READING      : begin

```

```

        next_state      = MOVE_TO_CACHE;
        move_from_mem    = 'b1;
        move_to_cache    = 'b1;
        stall            = 'b1;  /***/
        counter_enable= 'b1;

    end

MOVE_TO_CACHE : begin

    if(counter == 3'b100)
        begin
            next_state      = IDLE;
            read_from_cache = 'b1;
            stall           = 'b0;
            counter_enable  = 'b0;
            move_from_mem    = 'b0;
            move_to_cache    = 'b0;
        end
    else if(counter == 3'b011)
        begin
            next_state      = MOVE_TO_CACHE;
            read_from_cache = 'b0;
            stall           = 'b1;
            counter_enable  = 'b1;
            move_from_mem    = 'b0;
            move_to_cache    = 'b1;
        end
    else
        begin
            next_state      = MOVE_TO_CACHE;
            move_from_mem    = 'b1;
            move_to_cache    = 'b1;
            stall           = 'b1;
            counter_enable= 'b1;
        end
    end

WRITING : begin
    counter_enable='b1;

    if(check_Miss_hit )    // 1 hit      0 Miss
        begin
            write_in_cache = 'b1;
            write_in_mem    = 'b1;
            stall           = 'b1;
            next_state      =STALL;
        end
    else
        begin
            write_in_cache = 'b0;

```

```

        write_in_mem    ='b1;
        stall           ='b1;
        next_state      =STALL;
    end
end

STALL    : begin
    counter_enable  ='b1;

    if(counter == 'b100)
    begin
        stall='b0;
        write_in_cache='b0;
        write_in_mem='b0;
        next_state =IDLE;
        counter_enable  ='b0;
    end
    else
    begin
        stall='b1;
        write_in_cache='b0;
        write_in_mem='b1;
        next_state =STALL;
        counter_enable  ='b1;
    end
    end

default    : begin
    write_in_mem    ='b0;
    write_in_cache  ='b0;
    move_from_mem   ='b0;
    read_from_cache ='b0;
    stall           ='b0;
    counter_enable  ='b0;
    next_state      =IDLE;
    end
endcase
end
endmodule

```

## Cache Memory

```
module cache_Memory (
    input  wire      clk,rst,
    input  wire  [9:0] Word_address,
    input  wire  [31:0] data,
    input  wire  [31:0] Data_IN,
    input  wire      write_in_cache,read_from_cache,
    input  wire      move_to_cache,

    output reg      check_Miss_hit,
    output reg  [31:0] Data_Out
);

reg [31:0] cache_mem [0:127];
reg [3:0]  valid_tag [0:31];
reg [1:0]  move_count;
integer i,k;

always @(posedge clk or negedge rst )
    begin
        if(!rst)
            begin
                for (i=0;i<128;i=i+1)
                    begin
                        cache_mem[i]<='b0;
                    end
                for (k=0;k<32;k=k+1)
                    begin
                        valid_tag[k]<='b0;
                    end
                move_count <= 'b0;
            end

        else if (write_in_cache)
            begin
                cache_mem [Word_address[6:0]] <= Data_IN;
                valid_tag [Word_address[6:2]] <={1'b1,Word_address[9:7]};
            end

        else if (move_to_cache)
            begin
                cache_mem [{Word_address[6:2],move_count}] <= data;
                valid_tag [Word_address[6:2]] <={1'b1,Word_address[9:7]};
                move_count <= move_count +'b1;
            end

    end
end
```

```
always @(*)
begin
    if (valid_tag[Word_address[6:2]] == {1'b1 , Word_address [9:7]})
        begin
            check_Miss_hit ='b1;
        end
    else
        begin
            check_Miss_hit ='b0;
        end
end
always @(*) begin
    if (!rst) begin
        Data_Out='b0;

    end
    else if (read_from_cache)
        begin
            Data_Out = cache_mem [Word_address[6:0]];
        end
    else begin
        Data_Out='b0;
    end
end
endmodule
```

## Data Memory

```
module data_memory (
    input      wire      clk,rst,
    input      wire      [9:0] Word_address,
    input      wire      [31:0] Data_In,
    input      wire      write_in_mem,
    input      wire      move_to_cache,

    output     reg      [31:0]      data
);

    reg [31:0]  main_memory [0:1023];
    reg [1:0]   address_count;
    integer     i;

always@(posedge clk or negedge rst)
    begin
        if(!rst)
            begin
                for(i=0;i<1024;i=i+1)
                    main_memory[i] <='b0;
                    address_count  <='b0;
                    data            <='b0;
            end
        else
            begin
                if(write_in_mem)
                    begin
                        main_memory[Word_address] <= Data_In;
                        address_count             <='b0;
                    end
                else if (move_to_cache)
                    begin
                        address_count <=address_count+1;
                        data          <= main_memory[{Word_address[9:2],address_count}];
                    end
                else
                    begin
                        address_count <='b0;
                    end
            end
        end
    end

endmodule
```

## Cache Memory TOP

```
module cache_Memory_top (
    input  wire      clk,rst,
    input  wire      Mem_Write,Mem_Read,
    input  wire [9:0] Word_address,
    input  wire [31:0] Data_In,

    output wire      stall,
    output wire [31:0] Data_Out
) ;

/*****/
wire      check_Miss_hit;
wire      write_in_mem,write_in_cache;
wire      move_from_mem;
wire      move_to_cache;
wire      read_from_cache;

cache_controller u0(
    .clk(clk),
    .rst(rst),
    .Mem_Write(Mem_Write),
    .Mem_Read(Mem_Read),
    .check_Miss_hit(check_Miss_hit),

    .write_in_mem(write_in_mem),
    .write_in_cache(write_in_cache),
    .move_from_mem(move_from_mem),
    .move_to_cache(move_to_cache),
    .read_from_cache(read_from_cache),
    .stall(stall)
);

/*****/
wire [31:0] data;

cache_Memory u1(
    .clk(clk),
    .rst(rst),
    .Word_address(Word_address),
    .data(data),
    .Data_IN(Data_In),
    .write_in_cache(write_in_cache),
    .read_from_cache(read_from_cache),
    .move_to_cache(move_to_cache),

    .check_Miss_hit(check_Miss_hit),
    .Data_Out(Data_Out)
);
```

```
/******
```

```
data_memory u2(  
    .clk(clk),  
    .rst(rst),  
    .Word_address(Word_address),  
    .Data_In(Data_In),  
    .write_in_mem(write_in_mem),  
    .move_to_cache(move_from_mem),  
  
    .data(data)  
);
```

```
endmodule
```